

Jaypee University of Engineering & Technology, Guna

T-3 (Even Semester 2022)

18B11EC211 – ELECTRICAL SCIENCE

Maximum Duration: 2 Hours

Maximum Marks: 35

Notes:

1. This question paper has *seven* questions.
2. Write relevant answers only.
3. Do not write anything on question paper (Except your Er. No.).

Marks

Q1. Why silicon diode is preferred over germanium diode? Describe the V - I characteristics of P - N junction diode and calculate the current I in the circuit shown in Fig. 1 using the simplified equivalent model of the diode [05]

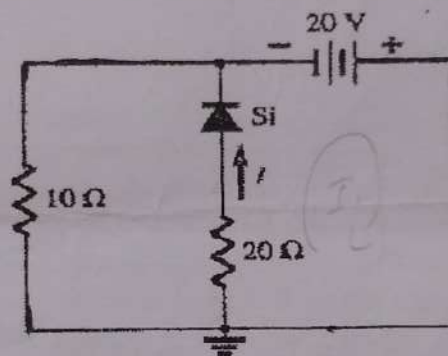


Fig. 1

Q2. Elaborate the clipper circuits. Determine and sketch v_o in the circuit shown in Fig.2 for positive and negative cycle of the given input v_i . [05]

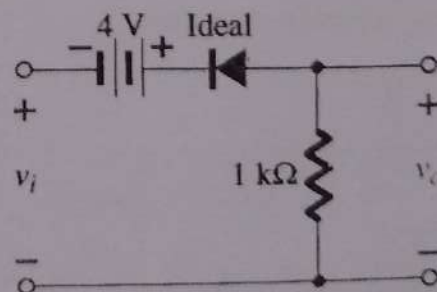
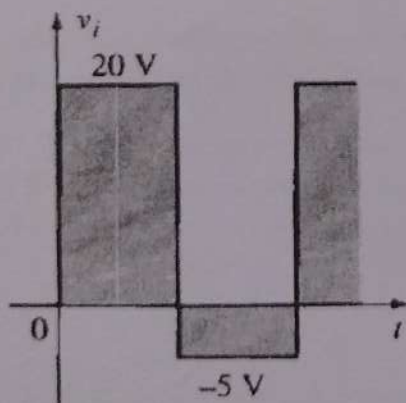


Fig. 2

- Q3. Explain the working principle of full wave bridge rectifier circuit and define their performance parameters. [05]
- Q4. What do you understand by bipolar junction transistor (BJT)? Explain various biasing conditions of BJT. [05]
- Q5. Define short circuit admittance parameters (Y-parameters) of two port network and find the Y-parameters for the circuit shown in Fig. 3. [05]

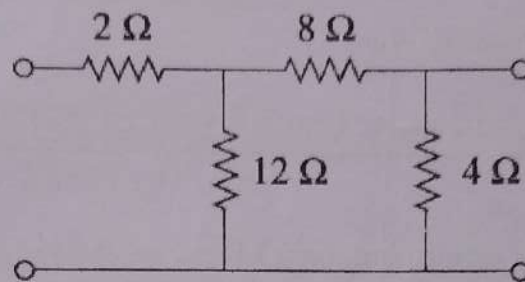


Fig. 3

- Q6. For the circuit shown in Fig. 4, calculate equivalent resistance R_{eq} looking from the terminal a - b and voltage V across $20\ \Omega$ resistance. [05]

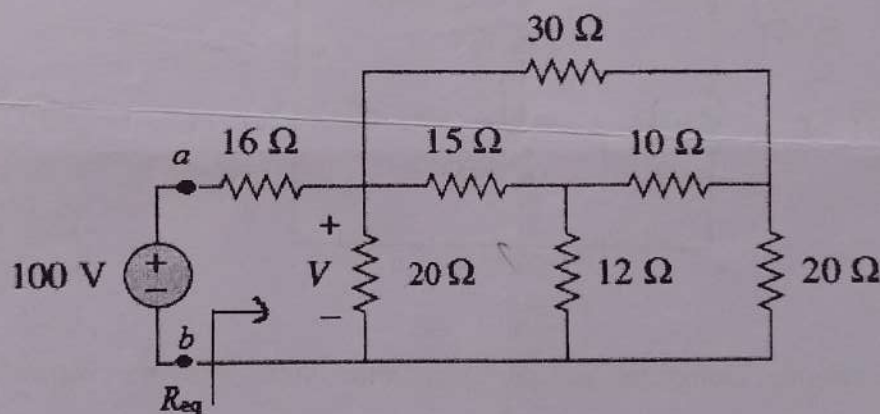


Fig. 4

- Q7. Write a short note on the followings. [05]
- Hybrid parameters (h-parameters)
 - Thevenin's Theorem