

Jaypee University of Engineering & Technology, Guna

T-1 (Even Semester 2022)
18B11EC211 - ELECTRICAL SCIENCE

Maximum Duration: 1 Hour


Maximum Marks: 15

Notes:


1. This question paper has *five* questions.
2. Write relevant answers only.
3. Do not write anything on question paper (Except your Er. No.).

Q1. What do you mean by active elements? Explain various types of dependent/controlled energy sources with the help of suitable example.

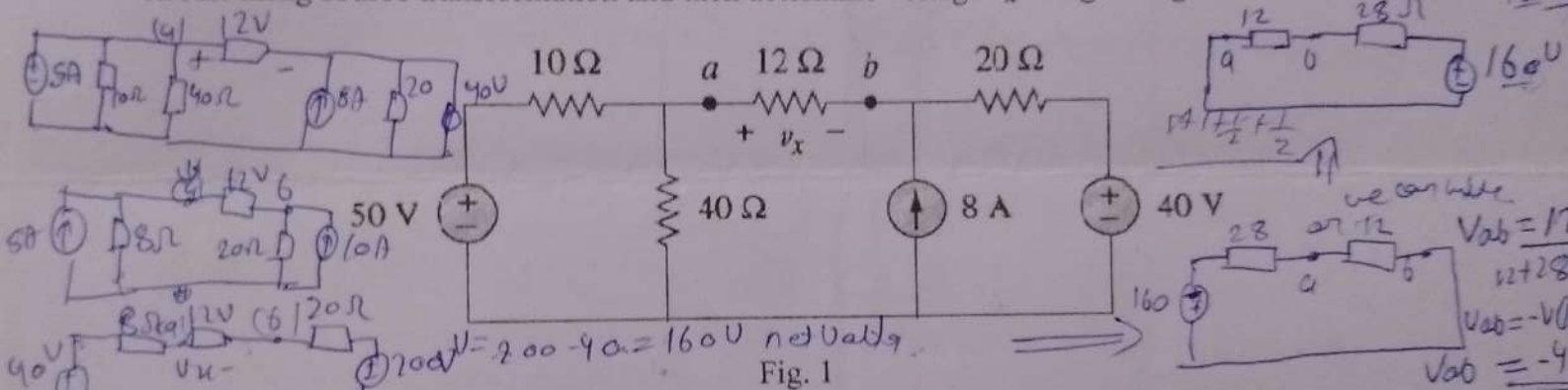Q2. Reduce the electrical circuit shown in Fig. 1 across $a-b$ into a single practical voltage source [03]
circuit using source transformation and then determine voltage v_x using voltage divider rule.



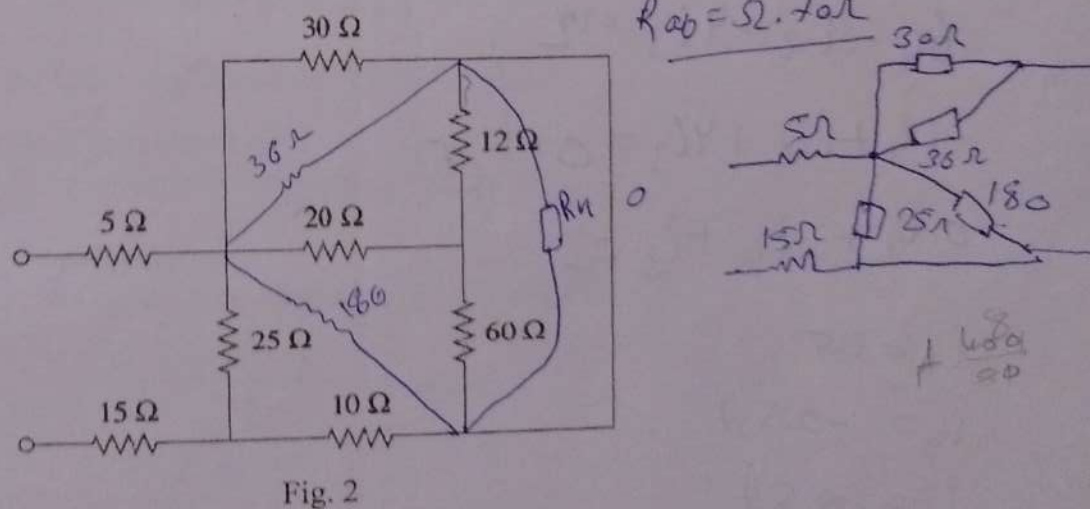Q3. Find the equivalent resistance at terminals $a-b$ of the circuit shown in Fig. 2.



$$12436 \text{ Re}_1 = \frac{30 \times 36}{168} = 6.43$$

- Q4. State the Kirchhoff's current law (KCL) and Kirchhoff's voltage law (KVL). Determine [03]
unknown voltages v_1 , v_2 , v_3 in the circuit shown in Fig. 3 using KVL.

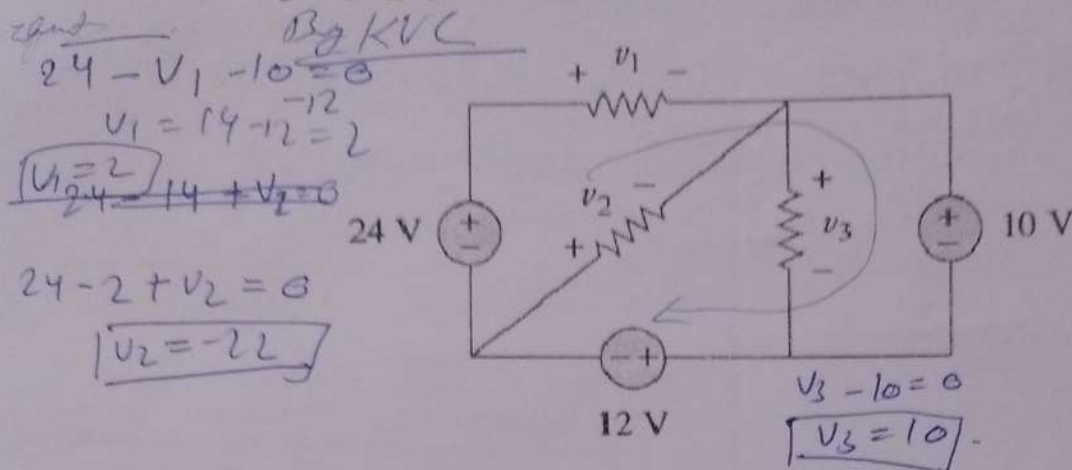


Fig. 3

- Q5. Use mesh analysis to calculate v_0 in the circuit shown in Fig. 4. [03]

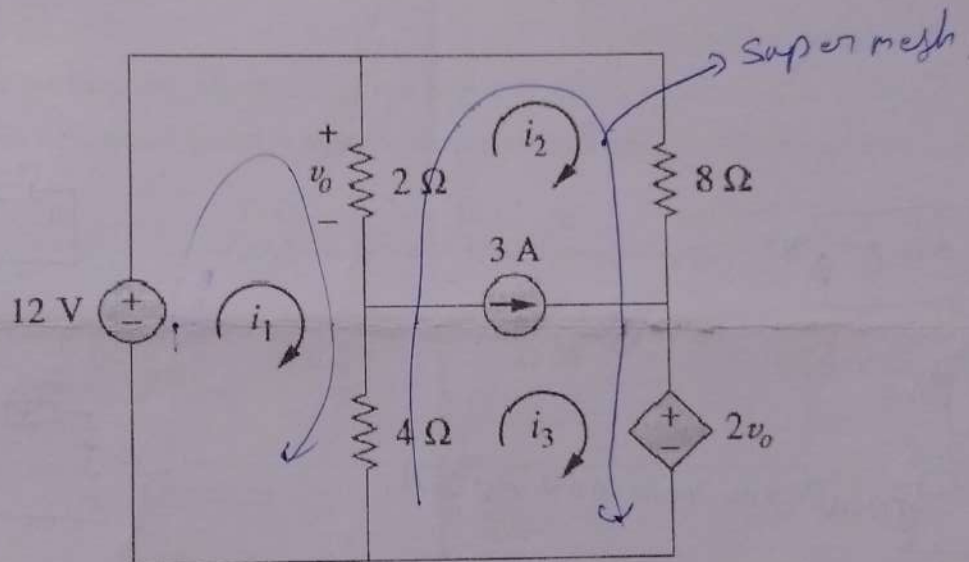


Fig. 4

$$\begin{cases} 6i_1 - 2i_2 - 4i_3 = 12 \\ -2i_1 + 6i_2 + 4i_3 = 0 \\ 0i_1 - i_2 + i_3 = 3 \end{cases}$$

$$i_1 = 3.5$$

$$i_2 = -0.5 \text{ A}$$

$$i_3 = 2.5 \text{ A}$$