

Academic Year 2021-22

Jaypee University of Engineering & Technology, Guna

T-2 (Even Semester 2022)
18B11EC212- ELECTRICAL CIRCUIT ANALYSIS

Maximum Marks: 25

Maximum duration: 1 Hour 30 Minutes

Notes:

1. This question paper has **six** questions.
2. Write relevant answers only.
3. Do not write anything on question paper.
4. Assume suitable data wherever necessary.

Q1. (a) Find out V_O in the network of Fig. (1) using nodal analysis.

[04]

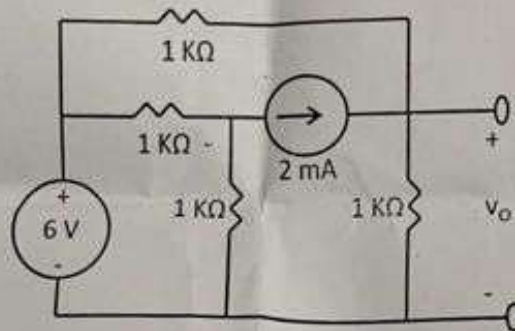


Fig. (1)

Q2. Calculate the voltage and current across 10Ω in the circuit as shown in Fig. (2) by using Thevenin's theorem. [05]

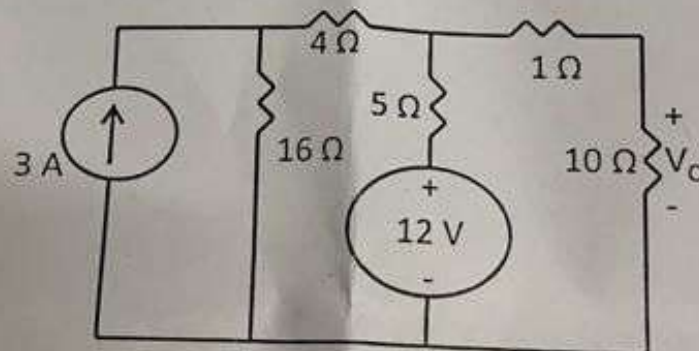


Fig. (2)

Determine the current in the x-y and a-b branch of Fig. (3) and verify the Reciprocity theorem.

[04]

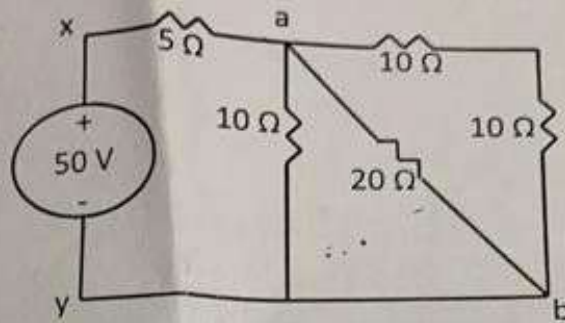


Fig. (3)

Q4.

State Thevenin's theorem with the help of suitable circuit diagram.

Q5.

In the circuit as shown in Fig. (4), the switch opens at $t = 0$. Find out $i_1(t)$ and $v_L(t)$ for $t > 0$. Also determine i_1 and v_L at $t = 1$ sec.

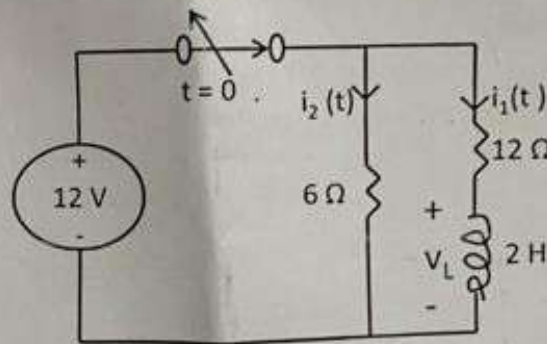


Fig. (4)

Q6.

Elaborate the different types of dependent sources along with the suitable circuit diagram.

[0